



Universitas Muhammadiyah Surakarta

Jl. A. Yani Tromol Pos I Pabelan Kartasura Telp (0271)717417, 719483 Fax.
(0271)715448 Surakarta 57102

UJIAN TENGAH SEMESTER GANJIL 2018/2019

MID SEMESTER EXAM OF ODD SEMESTER

FAKULTAS/FACULTY : TEKNIK/ENGINEERING			
JURUSAN/DEPARTMENT : Teknik Elektro/Electronic Engineering			
Mata Uji - Course	Elektronika Analog Lanjut	Hari / Tanggal – Day/Date	
Smt./Klas - Class	3/I	Jam ke - Session	
Penguji - Examiner	Dr. Ir. Bana Handaga, MT	Waktu - Duration	90 menit

Open Cheatsheet (1 sheet A4)

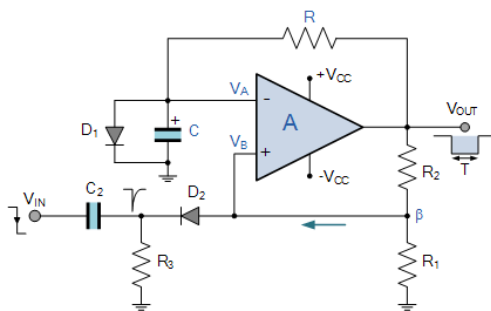


Figure-01

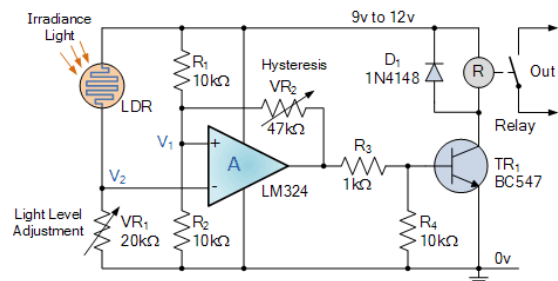


Figure-02

1. Describe the four ideal characteristics of an operational amplifier? (25%)
2. Design an inverting amplifier which has a voltage gain of 40dB? How much phase shift is on the output signal as compared with the input signal? (25%)
3. See Figure-01, what is the name of that circuit? How does the circuit work? If the formula to calculate the time constant is $T = RC \cdot \ln(1 + R_1/R_2)$, calculate the T of that circuit in seconds! Draw the output signal (25%)
4. See Figure-02, analyze how the circuit works? What is the main function of the OpAmp there? What are the conditions which can cause the relay to become active? (25%)